

AND STAPLE WHEN DONE


# RC Circuits and Diode Circuits

## Problem Set 2 for Tuesday Sept. 28


Gather together the four theory handouts that have been created and distributed. You will need them. Also get clean 8 1/2 x 11 paper, a pencil, and an eraser. High-quality work begins with assembling good tools, and taking pride in using them well.

These are directions not suggestions

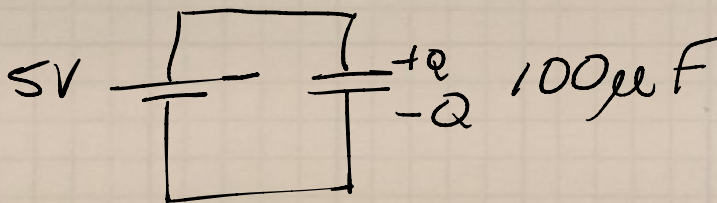1. A  $100\mu\text{F}$  capacitor has been charged up by a 5V power source.



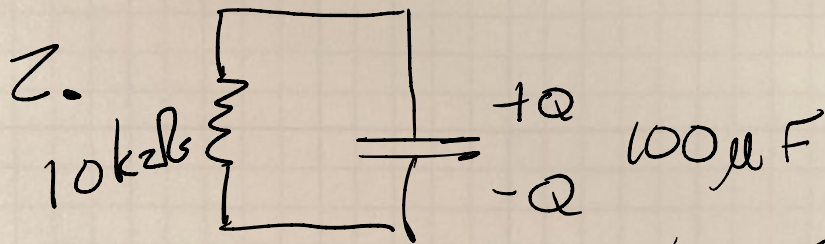- a. What is the charge  $Q$  on the positive plate of capacitor?
- b. What is the total charge on the capacitor?



The charged up capacitor from problem 1 is allowed to discharge through a 10kΩ resistor.

Make an accurate graph of  $Q(t)$ .

On the horizontal axis is time.

Have it go from 0 to 2.5 seconds with ticks every 0.5 seconds.

On the vertical axis is charge.


Have it go from 0.1 to 0.5 mC with ticks every 0.1 mC ↑  
with Coulombs

Before plotting your points, make and fill in a table, that will look something like this

$t$	0.0s	0.5s	1.0s	1.5s	etcetera
$Q(t)$	0.5mC	etcetera			

### 3. Diodes

Consider the following circuit!

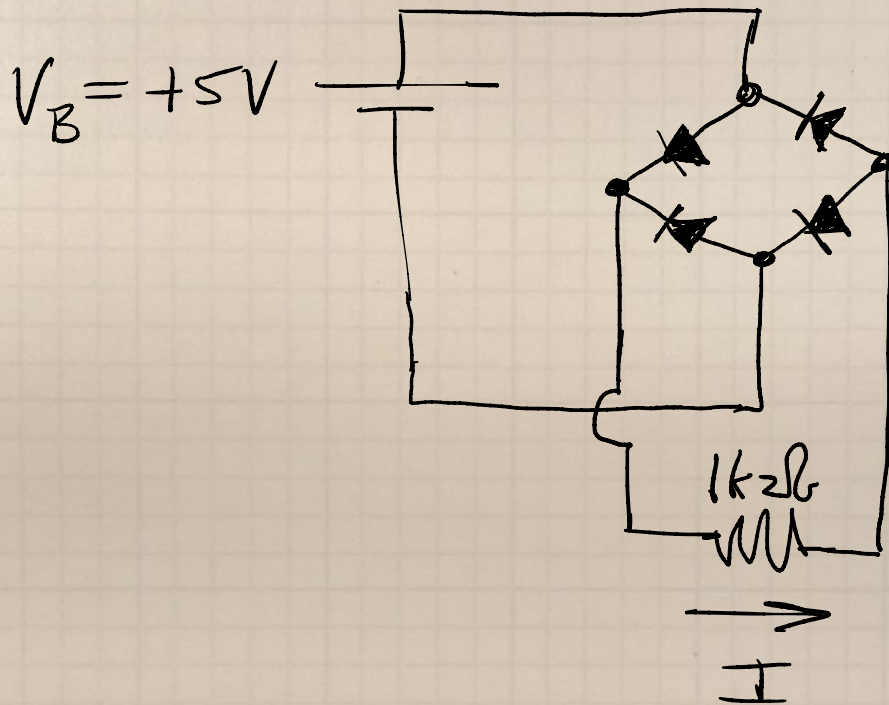

- How much current flows through the resistor?
- To the right (as drawn) or to the left?

Hints on next page




### HINTS FOR 3:

- \* You can assume the diodes are perfect — they either freely transmit current (if forward biased) or they completely block current.
- \* A diode that is completely blocking current can be removed from the circuit. Redraw the circuit with the diodes that are blocking current removed.
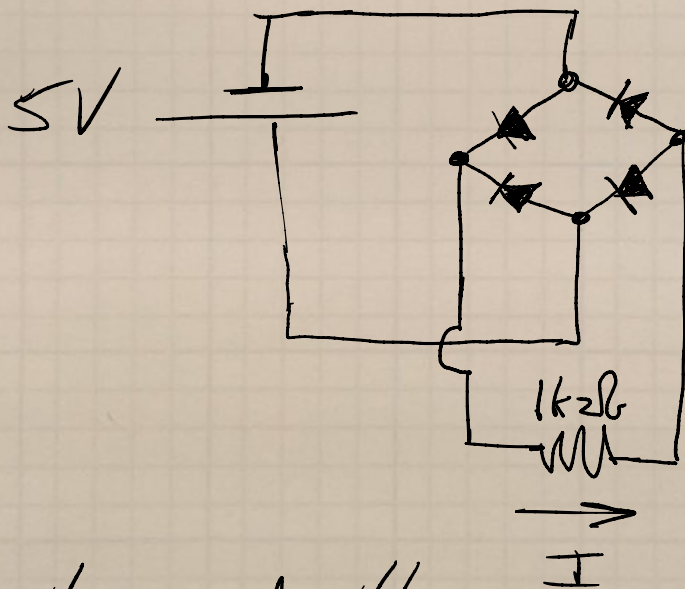
### 4. Diodes again

I have reversed the battery (no other changes):



4a. and 4b.

Answer the same questions as were asked in 3a. and 3b.

5. Compare your answers to 3b and 4b. Is this a possibly important use of four diodes?